

# Adaptive Power

## A Homemade USB Charging Solution


### Abstract

This paper presents "Adaptive Power," a homemade USB charging adapter designed to deliver 5-6 volts, suitable for charging various electronic devices, including cell phones, MP3 players, and cameras. This project involves the construction of an affordable and effective USB charger using commonly available electronic components. A comprehensive analysis of the design, implementation, and testing is provided, highlighting the potential applications and limitations of this innovative approach. The document elaborates on the practical construction and testing phases, ensuring a deep understanding of the circuit's operation.

**Keywords:** USB Charger, Bridge Rectifier, Voltage Regulator, DIY Electronics, Adaptive Power
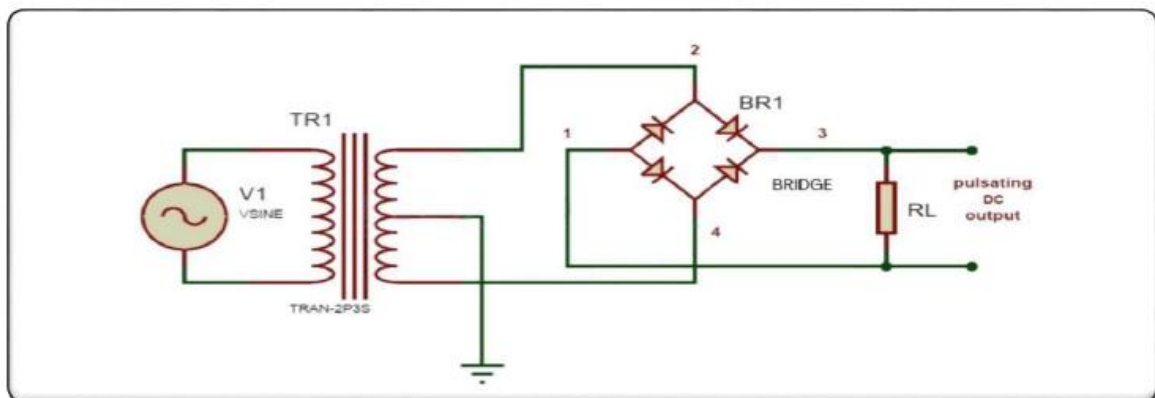
### 1. Introduction

The proliferation of portable electronic devices has significantly increased the demand for universal and affordable charging solutions. USB charging has emerged as a standard due to its versatility, simplicity, and compatibility across a broad range of devices. However, the availability of cost-effective charging solutions that can cater to diverse devices remains limited. Adaptive Power addresses this demand by providing an easily constructible homemade charging adapter. This project focuses on converting available resources into a functional and efficient charger, making it accessible to individuals with minimal technical expertise.



---

## 2. Objectives

The project aims to create a simple and inexpensive USB charger capable of delivering a stable 5-6 volts. The charger should:

- Be functional across various devices, ensuring compatibility.
  - Serve as an educational tool for understanding electronic circuit design and assembly.
  - Be easily replicable using readily available components.
- 

## 3. Methodology


### 3.1 Apparatus and Components

The construction of Adaptive Power requires the following components:

- Transformer (9V, 1A): Converts high AC voltage to a lower value suitable for rectification.
- Capacitor (25V, 100  $\mu$ F): Filters out AC ripples, ensuring smooth DC output.
- 1N4007 Diodes (4 units): Forms the bridge rectifier to convert AC to DC.
- Resistor (1K, 1/4W): Limits current and protects components.
- LED: Indicates operational status.
- PCB Board: Provides a platform for assembling components.
- USB Female Connector: Acts as the output interface for charging.
- 7805 Voltage Regulator: Maintains a steady 5V DC output.
- Wires and Soldering Tools: For connections and assembly.
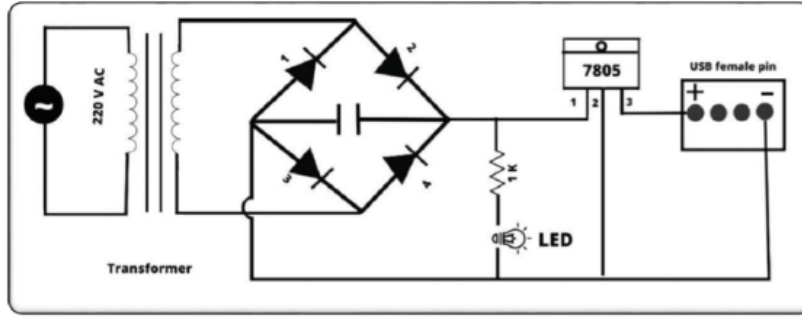
### 3.2 Circuit Design

The circuit design integrates a transformer, bridge rectifier, and voltage regulator to achieve a steady 5V DC output. The inclusion of capacitors ensures voltage stability, while the LED provides visual confirmation of operation. The USB connector facilitates the connection to various devices.



---

## 4. Implementation

### 4.1 Circuit Assembly

The assembly process involves:



1. Reducing the AC voltage from 220-230V to 9V using a transformer.
2. Converting AC to DC using a bridge rectifier composed of four 1N4007 diodes.
3. Filtering and stabilizing the DC voltage with a 25V, 100  $\mu$ F capacitor.
4. Regulating the DC voltage to 5V using a 7805 voltage regulator.
5. Integrating a USB connector to serve as the output interface.
6. Soldering the components onto a PCB board, ensuring secure connections.

### 4.2 Testing Procedure

The charger was tested with three devices—Samsung F23, MI Max, and Redmi 8a—to evaluate its charging performance. The following parameters were observed:

- Time taken to charge from 10% to 100%.
  - Voltage stability at various circuit points.
  - Compatibility with different battery capacities.
-

## 5. Results and Discussion

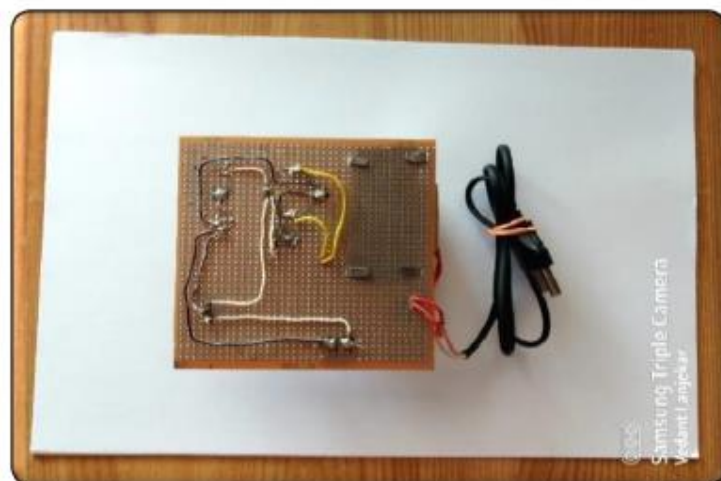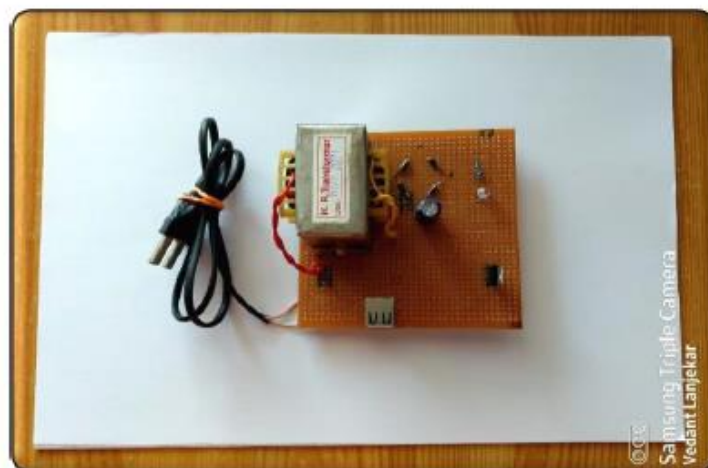

5.1 Observations

Device	Battery Capacity	10% Charge Time	Full Charge Time
Samsung F23	5000 mAh	25 mins	250 mins
Redmi 8a	4000 mAh	20 mins	200 mins
MI Max	3000 mAh	17 mins	170 mins

5.2 Voltage Analysis

Point	Expected Voltage	Measured Voltage
Transformer Input	220-230 AC	228 AC
Transformer Output	9 AC	10.35 AC
Rectifier Output	8.1 DC	9.31 DC
Voltage Regulator	5 DC	5.43 DC

The experimental results demonstrated that the charger meets the functional requirements. Voltage deviations remained within acceptable limits, ensuring reliable performance.

6. Pros and Cons

Pros:

- Cost-effective and easy-to-assemble components.
- Universally compatible with USB devices.
- Provides educational value in electronics and circuit assembly.

Cons:

- Limited to devices with moderate power requirements.
- Voltage fluctuations under high load conditions.
- Absence of advanced safety features, such as overcurrent protection.

## 7. Future Scope

The Adaptive Power project holds significant potential for future development. Possible enhancements include:

- Integration of advanced safety mechanisms, such as overcurrent and overheat protection.
  - Expansion into multi-port charging capabilities for simultaneous charging of multiple devices.
  - Optimization for higher efficiency, reducing energy loss during conversion.
  - Utilization of renewable energy sources, such as solar power, to make the charger eco-friendly.
  - Development of a compact and portable version for enhanced usability.
- 

## 7. Conclusion

Adaptive Power showcases the feasibility of constructing a homemade USB charging solution using readily available components. Despite its limitations, the project successfully achieves its objectives, providing a reliable and cost-effective charger for various devices. By addressing the identified drawbacks and leveraging its strengths, Adaptive Power can evolve into a more robust and versatile solution for modern charging needs.

---

## References

1. "Faraday's Law of Electromagnetic Induction," Byju's. <https://byjus.com/physics/faradays-law/>
  2. "Connector Definitions," TechTarget. <https://www.techtarget.com/>
-